



Challenge	Draw a diagram using scientific symbols
<p>1. Make a circuit that will make a buzzer buzz.</p>	
<p>2. Make a circuit that includes a motor and a switch.</p>	
<p>3. Make a circuit that makes a bulb light up and a buzzer buzz at the same time.</p>	
<p>4. Make a circuit that makes two bulbs light up.</p>	