

Activity



Challenge	Draw a diagram using scientific symbols
1. Make a circuit that will make a buzzer buzz.	
2. Make a circuit that includes a motor and a switch.	
3. Make a circuit that makes a bulb light up and a buzzer buzz at the same time.	
4. Make a circuit that makes two bulbs light up.	

