



Challenge

Now, make up **two** of your own circuits.
Predict if they will work and then **test** them.

Circuit Diagram	Do you think it will work? Explain your answer.	Did it work?



www.grammarsaurus.co.uk



Challenge

Now, make up **two** of your own circuits.
Predict if they will work and then **test** them.

Circuit Diagram	Do you think it will work? Explain your answer.	Did it work?



www.grammarsaurus.co.uk