

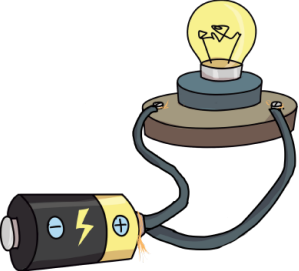
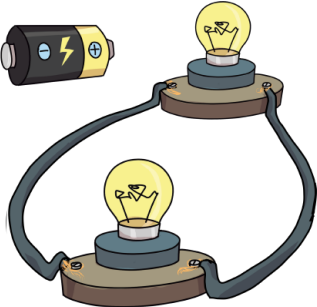
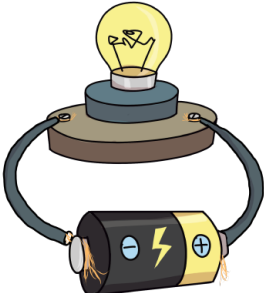


Activity

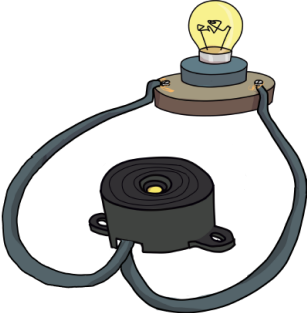

Circuit	Will the bulb light up? Explain your answer.
	<div> Yes No </div> <div> <input type="checkbox"/> <input type="checkbox"/> </div> <hr/> <hr/>
	<div> Yes No </div> <div> <input type="checkbox"/> <input type="checkbox"/> </div> <hr/> <hr/>
	<div> Yes No </div> <div> <input type="checkbox"/> <input type="checkbox"/> </div> <hr/> <hr/>
	<div> Yes No </div> <div> <input type="checkbox"/> <input type="checkbox"/> </div> <hr/> <hr/>
	<div> Yes No </div> <div> <input type="checkbox"/> <input type="checkbox"/> </div> <hr/> <hr/>

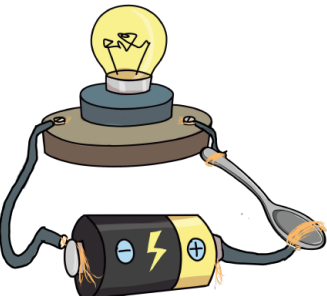