

Next step



One of the bulbs is missing from the string of **Christmas tree lights**. If they are plugged into the mains electricity, will the lights work? Explain your answer.



www.grammarsaurus.co.uk

Next step



One of the bulbs is missing from the string of **Christmas tree lights**. If they are plugged into the mains electricity, will the lights work? Explain your answer.



www.grammarsaurus.co.uk

Next step



One of the bulbs is missing from the string of **Christmas tree lights**. If they are plugged into the mains electricity, will the lights work? Explain your answer.



www.grammarsaurus.co.uk