

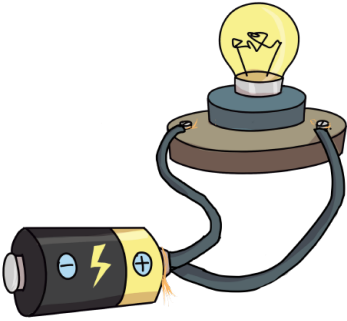


Activity

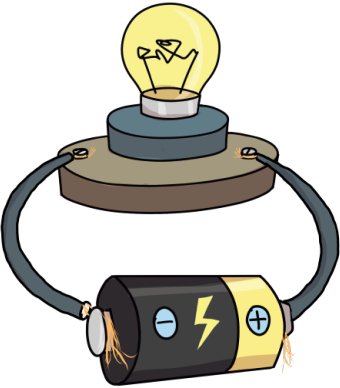

Circuit	Will the bulb light up? Explain your answer.
	<div><div>Yes</div><div>No</div></div> <div><input type="checkbox"/><input type="checkbox"/></div> <div><hr/><hr/><hr/><hr/></div>
	<div><div>Yes</div><div>No</div></div> <div><input type="checkbox"/><input type="checkbox"/></div> <div><hr/><hr/><hr/><hr/></div>
	<div><div>Yes</div><div>No</div></div> <div><input type="checkbox"/><input type="checkbox"/></div> <div><hr/><hr/><hr/><hr/></div>

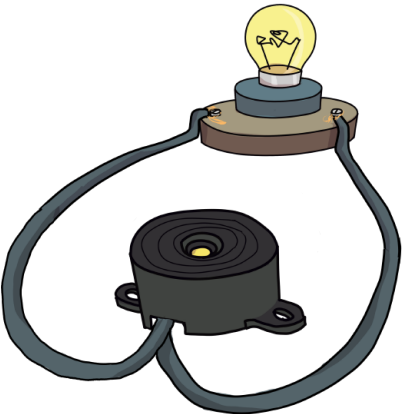