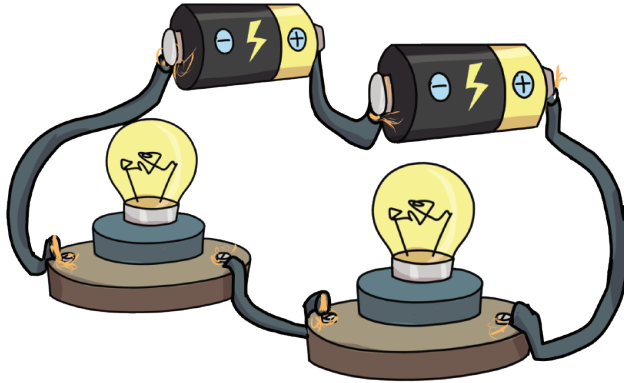


Challenge

Jamie builds the **circuit** below. The bulbs do **light up**.



1. Draw a **circuit diagram** for Jamie's circuit in the space below.

2. Jamie wants to **change** his circuit so that the two bulbs are brighter.

He can use any other **equipment**.

Suggest **TWO ways** Jamie can make his two bulbs brighter.

1. _____

2. _____

