

# Activity



Make a circuit that includes	Draw a diagram of the circuit	Total voltage of batteries	Bulb brightness
1 battery 2 wires 1 bulb			dim / normal / bright
1 battery 3 wires 2 bulbs			dim / normal / bright
2 batteries 3 wires 1 bulb			dim / normal / bright
2 batteries 4 wires 2 bulbs			dim / normal / bright
2 batteries 5 wires 3 bulbs			dim / normal / bright
3 batteries 6 wires 3 bulbs			dim / normal / bright

