

Next Step

Prediction

1. What would happen to **the volume** of a buzzer if you **increased** the voltage of the cells in **the circuit**? Explain your answer.

2. What would happen to **the volume** of a buzzer if you **decreased** the voltage of the cells in **the circuit**? Explain your answer.



www.grammarsaurus.co.uk

Next Step

Prediction

1. What would happen to **the volume** of a buzzer if you **increased** the voltage of the cells in **the circuit**? Explain your answer.

2. What would happen to **the volume** of a buzzer if you **decreased** the voltage of the cells in **the circuit**? Explain your answer.



www.grammarsaurus.co.uk