

# Activity



Make a circuit that includes	Draw a diagram of the circuit	Total voltage of batteries	What happened to the bulb?
1 battery 2 wires 1 bulb			
1 battery 3 wires 2 bulbs			
2 batteries 3 wires 1 bulb			
2 batteries 4 wires 2 bulbs			
2 batteries 5 wires 3 bulbs			
3 batteries 6 wires 3 bulbs			

